

# ELL101: Introduction to Electrical Engineering

Madhusudan Singh, Manan Suri, Saif K. Mohammad, Shubhendu  
Bhasin and A. P. Prathosh

IIT Delhi

Winter 2021

## Lecture 14: Zener diodes, diode circuits and rectification

# Recap


Materials used here are bound by Fair Use for educational purpose.

- Calculation of electron and hole carrier densities from three-dimensional density of states and Fermi function. Effective mass. Fermi level.
- Intrinsic carrier concentration ( $3k_B T$  approximation). Intrinsic energy level. Position of the Fermi level as a signature of doping. Peculiarity of physical units used in semiconductor physics.
- Carrier mobility and electric field dependence of carrier velocities. Ohm's law. Conductivity. Resistivity.
- Reading semiconductor properties tables.
- Carrier generation - thermal and optical. Generation rates. Low light level approximation. Recombination time constant.
- Carrier recombination. Electroluminescence.
- pn junctions. Formation of depletion region. Bending of bands. Diffusion and drift. Diode equation. Importance of reporting current density rather than current.
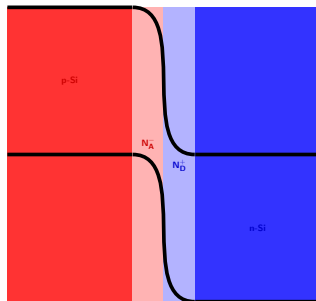
# Zener diodes

Materials used here are bound by Fair Use for educational purpose.


- Special type of diodes - very heavy doping on both sides.


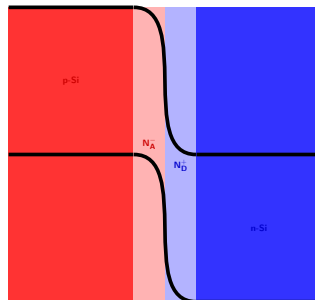
# Zener diodes

Materials used here are bound by Fair Use for educational purpose.

- Special type of diodes - very heavy doping on both sides.
- Depletion region narrows, and bands nearly line up. Tunneling is possible at high enough reverse bias.



$$J = qvn \exp \left[ -\frac{4}{3q\hbar E} \sqrt{2m^* \mathcal{E}_g^3} \right]$$

Tunnel probability


# Zener diodes

Materials used here are bound by Fair Use for educational purpose.

- Special type of diodes - very heavy doping on both sides.
- Depletion region narrows, and bands nearly line up. Tunneling is possible at high enough reverse bias.
- “Designer” breakdown. Reverse bias current rises rapidly at a certain voltage. Can largely maintain that voltage regardless of current.

$$J = qvn \exp \left[ -\frac{4}{3q\hbar E} \sqrt{2m^* \mathcal{E}_g^3} \right]$$


Tunnel probability

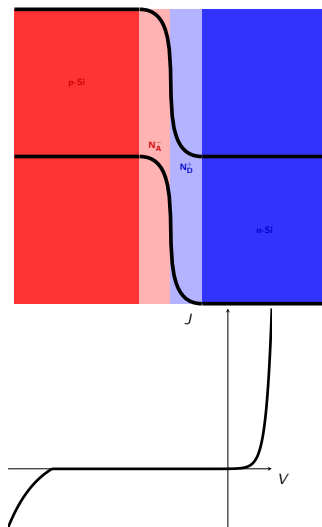
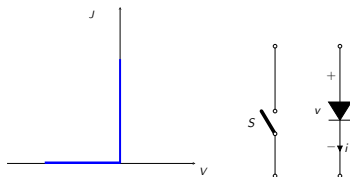
# The diode as an ideal switch

Materials used here are bound by Fair Use for educational purpose.


- Zero resistance in forward bias.
- Infinite resistance in reverse bias.


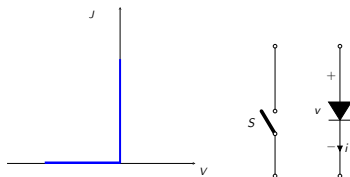
# The diode as an ideal switch

Materials used here are bound by Fair Use for educational purpose.

- Zero resistance in forward bias.
- Infinite resistance in reverse bias.
- This acts like an ideal switch.





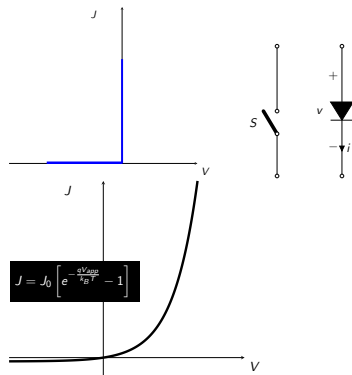
# The diode as an ideal switch

Materials used here are bound by Fair Use for educational purpose.


- Zero resistance in forward bias.
- Infinite resistance in reverse bias.
- This acts like an ideal switch.
- Differs from an ideal diode.  
Exponential relationship.


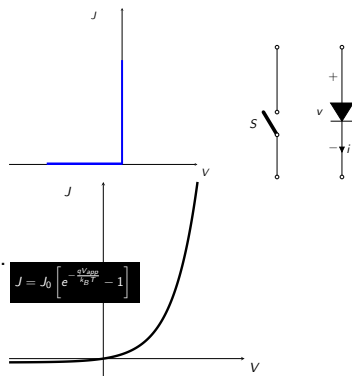
# The diode as an ideal switch

Materials used here are bound by Fair Use for educational purpose.


- Zero resistance in forward bias.
- Infinite resistance in reverse bias.
- This acts like an ideal switch.
- Differs from an ideal diode.  
Exponential relationship.
- Si: 0.7 V. Ge: 0.5 V. Knee voltage.


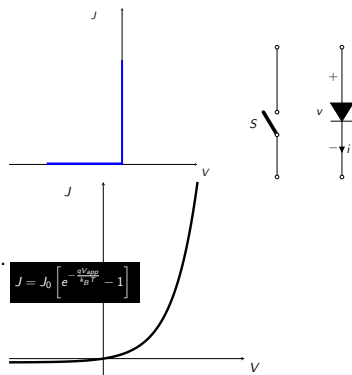
# The diode as an ideal switch


Materials used here are bound by Fair Use for educational purpose.

- Zero resistance in forward bias.
- Infinite resistance in reverse bias.
- This acts like an ideal switch.
- Differs from an ideal diode. Exponential relationship.
- Si: 0.7 V. Ge: 0.5 V. Knee voltage.
- Several applications:
  - AC-DC conversion: rectifier.
  - Peak detection, DC restoration: clamper.
  - Wave shaping: clipper.


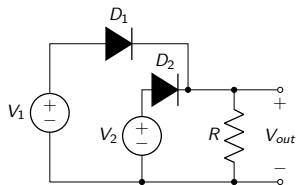
# Worked example 1


Materials used here are bound by Fair Use for educational purpose.



- The IC employs Si technology with junction potential 0.7 V.  $V_1 = 5V$  and  $V_2 = 0V$ . Find  $V_{out}$ .
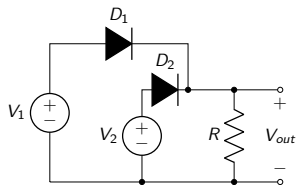
# Worked example 1


Materials used here are bound by Fair Use for educational purpose.



- The IC employs Si technology with junction potential 0.7 V.  $V_1 = 5V$  and  $V_2 = 0V$ . Find  $V_{out}$ .
- Biasing of the diodes is determined by  $V_{out}$ . Three possible cases:
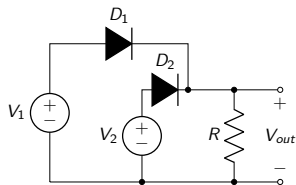
# Worked example 1


Materials used here are bound by Fair Use for educational purpose.



- The IC employs Si technology with junction potential  $0.7\text{ V}$ .  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Find  $V_{out}$ .
- Biasing of the diodes is determined by  $V_{out}$ . Three possible cases:
  - 1  $0 < V_{out} < 5$ :  $D_1$  is FB and  $D_2$  is RB.  
 $V_{out} = V_1 - 0.7 = 4.3\text{ V}$ .
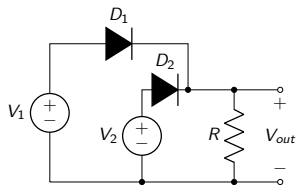
# Worked example 1


Materials used here are bound by Fair Use for educational purpose.



- The IC employs Si technology with junction potential  $0.7\text{ V}$ .  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Find  $V_{out}$ .
- Biasing of the diodes is determined by  $V_{out}$ . Three possible cases:
  - 1  $0 < V_{out} < 5$ :  $D_1$  is FB and  $D_2$  is RB.  
 $V_{out} = V_1 - 0.7 = 4.3\text{ V}$ .
  - 2  $V_{out} > 5$ : Both diodes are RB.  $V_{out} > 5\text{ V}$  and  $V_{out} > 0\text{ V}$ . No current in  $R$ . Contradiction.
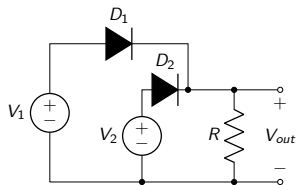
# Worked example 1

Materials used here are bound by Fair Use for educational purpose.




- The IC employs Si technology with junction potential  $0.7\text{ V}$ .  $V_1 = 5\text{ V}$  and  $V_2 = 0\text{ V}$ . Find  $V_{out}$ .
- Biasing of the diodes is determined by  $V_{out}$ . Three possible cases:
  - 1  $0 < V_{out} < 5$ :  $D_1$  is FB and  $D_2$  is RB.  $V_{out} = V_1 - 0.7 = 4.3\text{ V}$ .
  - 2  $V_{out} > 5$ : Both diodes are RB.  $V_{out} > 5\text{ V}$  and  $V_{out} > 0\text{ V}$ . No current in  $R$ . Contradiction.
  - 3  $V_{out} < 0$ : Both diodes are FB.  $V_{out}$  is overspecified.


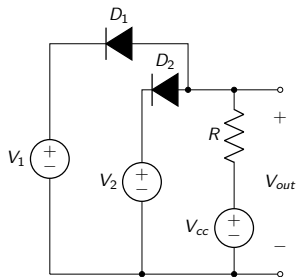
## Worked example 2


Materials used here are bound by Fair Use for educational purpose.



- Si technology with junction potential  $0.7\text{ V}$ .  $V_1 = 5\text{ V}$ ,  $V_2 = 0\text{ V}$  and  $V_{cc} = 6\text{ V}$ . Find  $V_{out}$ .
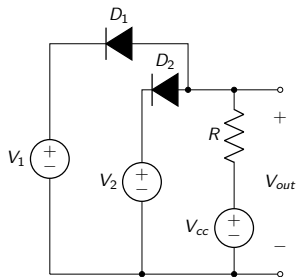
## Worked example 2


Materials used here are bound by Fair Use for educational purpose.



- Si technology with junction potential 0.7 V.  $V_1 = 5V$ ,  $V_2 = 0V$  and  $V_{cc} = 6V$ . Find  $V_{out}$ .
- Cases:
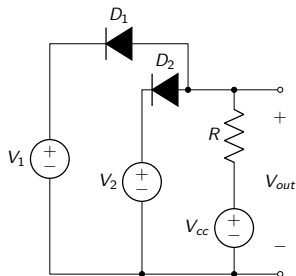
## Worked example 2


Materials used here are bound by Fair Use for educational purpose.



- Si technology with junction potential 0.7 V.  $V_1 = 5V$ ,  $V_2 = 0V$  and  $V_{cc} = 6V$ . Find  $V_{out}$ .
- Cases:
  - ①  $D_1$  and  $D_2$  are FB:  $5 < V_{out} < 6$ :  $V_{out}$  is overspecified.
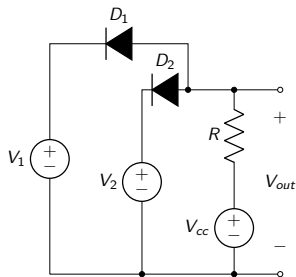
## Worked example 2


Materials used here are bound by Fair Use for educational purpose.



- Si technology with junction potential 0.7 V.  $V_1 = 5V$ ,  $V_2 = 0V$  and  $V_{cc} = 6V$ . Find  $V_{out}$ .
- Cases:
  - 1  $D_1$  and  $D_2$  are FB:  $5 < V_{out} < 6$ :  $V_{out}$  is overspecified.
  - 2  $D_1$  and  $D_2$  are RB.  $V_{out} < 0$ : Current through the resistor needs to be large enough to counter  $V_{cc}$ . Contradiction.
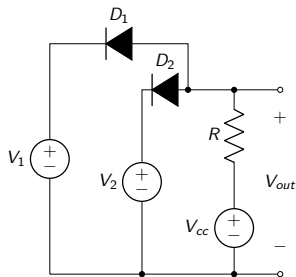
## Worked example 2


Materials used here are bound by Fair Use for educational purpose.



- Si technology with junction potential 0.7 V.  $V_1 = 5V$ ,  $V_2 = 0V$  and  $V_{cc} = 6V$ . Find  $V_{out}$ .
- Cases:
  - 1  $D_1$  and  $D_2$  are FB:  $5 < V_{out} < 6$ :  $V_{out}$  is overspecified.
  - 2  $D_1$  and  $D_2$  are RB.  $V_{out} < 0$ : Current through the resistor needs to be large enough to counter  $V_{cc}$ . Contradiction.
  - 3  $D_1$  is FB ( $V_{out} > 5V$ ) and  $D_2$  is RB ( $V_{out} < 0V$ ). Contradiction.
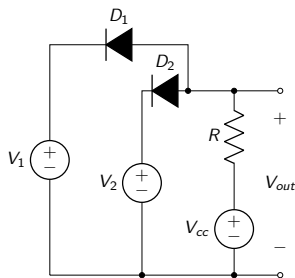
## Worked example 2

Materials used here are bound by Fair Use for educational purpose.




- Si technology with junction potential 0.7 V.  $V_1 = 5V$ ,  $V_2 = 0V$  and  $V_{cc} = 6V$ . Find  $V_{out}$ .

- Cases:

- 1  $D_1$  and  $D_2$  are FB:  $5 < V_{out} < 6$ :  $V_{out}$  is overspecified.
- 2  $D_1$  and  $D_2$  are RB.  $V_{out} < 0$ : Current through the resistor needs to be large enough to counter  $V_{cc}$ . Contradiction.
- 3  $D_1$  is FB ( $V_{out} > 5V$ ) and  $D_2$  is RB ( $V_{out} < 0V$ ). Contradiction.
- 4  $D_1$  is RB ( $V_{out} < 5V$ ) and  $D_2 > 0V$ . Possible.  $V_{out} = 0 + 0.7 = 0.7V$
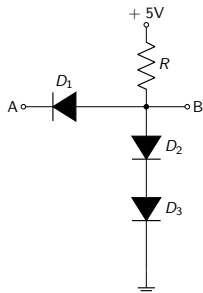
## Worked example 3


Materials used here are bound by Fair Use for educational purpose.



- Si technology. Find  $V_B$  for  $V_A = -1, 0, 1$  and  $2V$
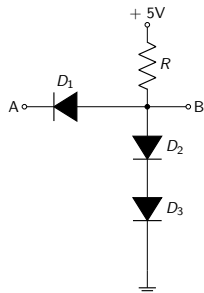
## Worked example 3

Materials used here are bound by Fair Use for educational purpose.



- Si technology. Find  $V_B$  for  $V_A = -1, 0, 1$  and  $2V$


$D_2, D_3$ : FB

$D_2, D_3$ : RB


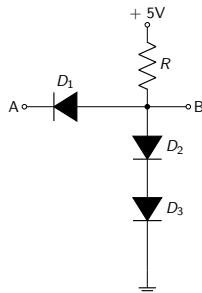
# Worked example 3

Materials used here are bound by Fair Use for educational purpose.




- Si technology. Find  $V_B$  for  $V_A = -1, 0, 1$  and  $2V$

	$D_2, D_3$ : FB	$D_2, D_3$ : RB
$D_1$ : RB	$V_A > V_B > 0,$ $V_B = 0.7 + 0.7 =$ $1.4V$	$V_B < \min(V_A, 0),$ $V_B = ?$
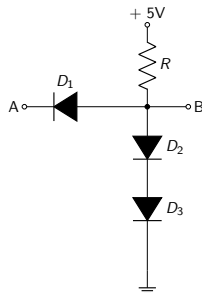
# Worked example 3

Materials used here are bound by Fair Use for educational purpose.



- Si technology. Find  $V_B$  for  $V_A = -1, 0, 1$  and  $2V$

	$D_2, D_3$ : FB	$D_2, D_3$ : RB
$D_1$ : RB	$V_A > V_B > 0$ , $V_B = 0.7 + 0.7 = 1.4V$	$V_B < \min(V_A, 0)$ , $V_B = ?$
$D_1$ : FB	$V_B > V_A$ , $V_B > 0$ , $V_B = \min(V_A + 0.7, 1.4)$	$V_A < V_B < 0$ $V_B = V_A + 0.7$


# Rectification

Materials used here are bound by Fair Use for educational purpose.

- Conversion of an AC current to unidirectional pulsating current by using an asymmetric device (for instance a diode).
- Two types:
  - 1 Half-wave rectifier: uses only half of an AC signal.
  - 2 Full-wave rectifier: uses both halves of an AC signal.


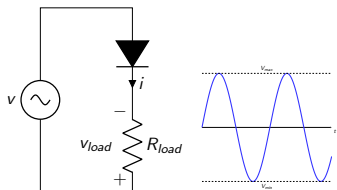
# Half-Wave Rectifier

Materials used here are bound by Fair Use for educational purpose.



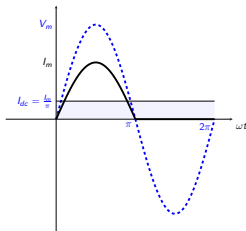
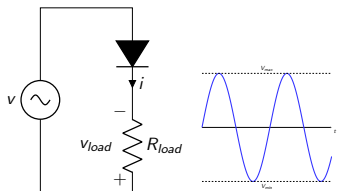
# Half-Wave Rectifier

Materials used here are bound by Fair Use for educational purpose.


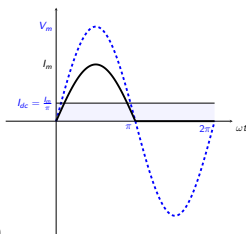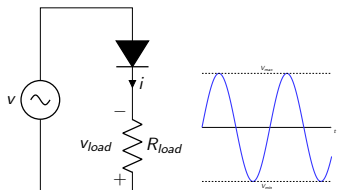
# Half-Wave Rectifier



Materials used here are bound by Fair Use for educational purpose.



- The DC value of current can be estimated using ideal switch behaviour for the diode.
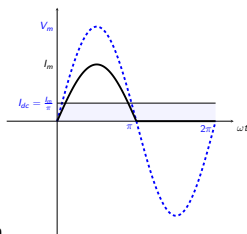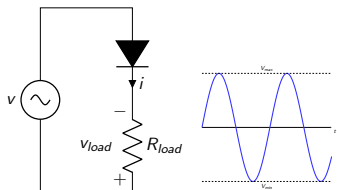
# Half-Wave Rectifier

Materials used here are bound by Fair Use for educational purpose.





- The DC value of current can be estimated using ideal switch behaviour for the diode.
- It is the time average over one full cycle.

$$i = \frac{v}{R_{load}} = \begin{cases} \frac{V_m \sin \omega t}{R_{load}} & 0 \leq \omega t \leq \pi \\ 0 & \pi \leq \omega t < 2\pi \end{cases}$$
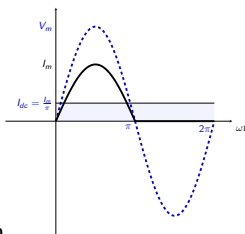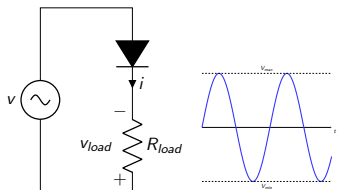
# Half-Wave Rectifier

Materials used here are bound by Fair Use for educational purpose.



- The DC value of current can be estimated using ideal switch behaviour for the diode.

$$i = \frac{v}{R_{load}} = \begin{cases} \frac{V_m \sin \omega t}{R_{load}} & 0 \leq \omega t \leq \pi \\ 0 & \pi \leq \omega t < 2\pi \end{cases}$$

- It is the time average over one full cycle.
- Second half cycle drops out. Approx. 32% for both current and load voltage.

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i d(\omega t) = \frac{1}{2\pi} \int_0^{\pi} \frac{V_m \sin \omega t}{R_{load}} d(\omega t)$$

$$I_{dc} = \frac{V_m}{\pi R_{load}} \equiv \frac{I_m}{\pi}; \text{ and, } V_{dc} = \frac{V_m}{\pi}$$



# Discussion

Materials used here are bound by Fair Use for educational purpose.

- RMS value of load voltage ( $v_{load}$ ) is given by

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)} = \frac{V_m}{2}$$

# Discussion

Materials used here are bound by Fair Use for educational purpose.

- RMS value of load voltage ( $v_{load}$ ) is given by

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)} = \frac{V_m}{2}$$

- The rectification efficiency can be defined as the squared ratio of DC voltage to the RMS value:

$$\eta = \left( \frac{V_{dc}}{V_{rms}} \right)^2 = \frac{4}{\pi^2} \approx 40\%$$

# Discussion

Materials used here are bound by Fair Use for educational purpose.

- RMS value of load voltage ( $v_{load}$ ) is given by

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)} = \frac{V_m}{2}$$

- The rectification efficiency can be defined as the squared ratio of DC voltage to the RMS value:

$$\eta = \left( \frac{V_{dc}}{V_{rms}} \right)^2 = \frac{4}{\pi^2} \approx 40\%$$

- Maximum reverse voltage experienced by the diode is called the peak inverse voltage. Must not exceed breakdown voltage. It is approx. peak value of  $v$ .

# Discussion

Materials used here are bound by Fair Use for educational purpose.

- RMS value of load voltage ( $v_{load}$ ) is given by

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)} = \frac{V_m}{2}$$

- The rectification efficiency can be defined as the squared ratio of DC voltage to the RMS value:

$$\eta = \left( \frac{V_{dc}}{V_{rms}} \right)^2 = \frac{4}{\pi^2} \approx 40\%$$

- Maximum reverse voltage experienced by the diode is called the peak inverse voltage. Must not exceed breakdown voltage. It is approx. peak value of  $v$ .
- Half-wave rectification is considered to be insufficient for most applications as it loses half the cycle, and output is hard to filter.

# Discussion

Materials used here are bound by Fair Use for educational purpose.

- RMS value of load voltage ( $v_{load}$ ) is given by

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)} = \frac{V_m}{2}$$

- The rectification efficiency can be defined as the squared ratio of DC voltage to the RMS value:

$$\eta = \left( \frac{V_{dc}}{V_{rms}} \right)^2 = \frac{4}{\pi^2} \approx 40\%$$

- Maximum reverse voltage experienced by the diode is called the peak inverse voltage. Must not exceed breakdown voltage. It is approx. peak value of  $v$ .
- Half-wave rectification is considered to be insufficient for most applications as it loses half the cycle, and output is hard to filter.
- Application: two position lamp dimmer switch.