

# ELL101: Introduction to Electrical Engineering

Madhusudan Singh, Manan Suri, Saif K. Mohammad, Shubhendu  
Bhasin and A. P. Prathosh

IIT Delhi

Winter 2021

## Lecture 15: Rectification and waveshaping circuits

# Recap


Materials used here are bound by Fair Use for educational purpose.

- Zener diodes. Effect of heavy doping. Tunneling current. Designed breakdown at a specific reverse voltage. Voltage regulation applications.
- The diode as an ideal switch. Abuse of terminology: an ideal switch is not an ideal diode. Knee voltage for Si and Ge. Applications of ideal switches.
- Worked examples of diode circuits. Need for care in identifying the polarity of diode in biasing.
- Half-wave rectification. DC current, load and RMS voltage. Rectification efficiency estimation. Peak inverse voltage. Example of an application.

# Full-Wave Rectifiers

Materials used here are bound by Fair Use for educational purpose.

- Bridge rectifier:

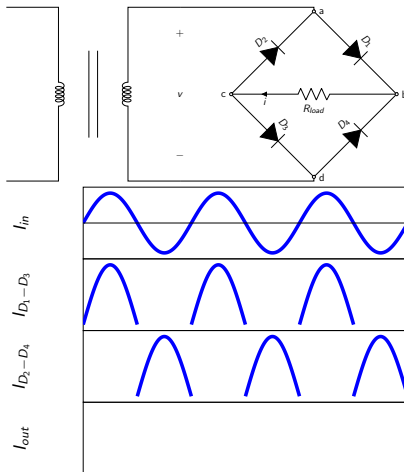


# Full-Wave Rectifiers

Materials used here are bound by Fair Use for educational purpose.

- Bridge rectifier:

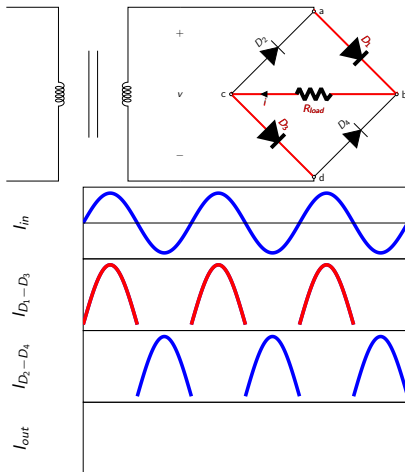- +ve 1/2 cycle:  $D_1$  and  $D_3$  conduct: a-b-c-d.




# Full-Wave Rectifiers

Materials used here are bound by Fair Use for educational purpose.

- Bridge rectifier:

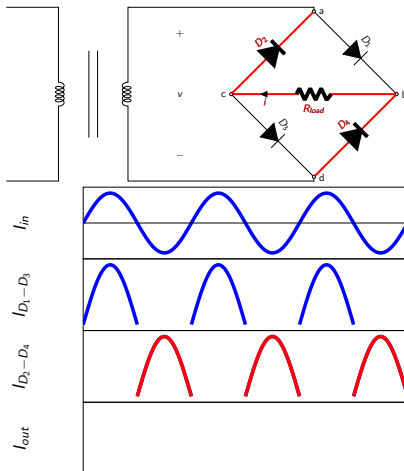- +ve 1/2 cycle:  $D_1$  and  $D_3$  conduct: a-b-c-d.
- -ve 1/2 cycle:  $D_2$  and  $D_4$  conduct: d-b-c-a.




# Full-Wave Rectifiers

Materials used here are bound by Fair Use for educational purpose.
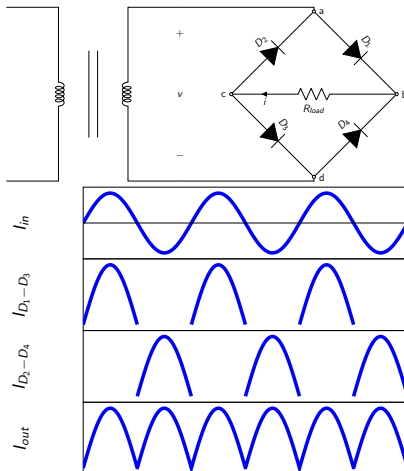
## • Bridge rectifier:

- +ve 1/2 cycle:  $D_1$  and  $D_3$  conduct: a-b-c-d.
- -ve 1/2 cycle:  $D_2$  and  $D_4$  conduct: d-b-c-a.
- $V_{DC} = \frac{2}{\pi} V_m \approx 64\% V_m$ .  
Peak-inverse voltage seen by each diode =  $V_m$ .



# Full-Wave Rectifiers


Materials used here are bound by Fair Use for educational purpose.

- Bridge rectifier:

- +ve 1/2 cycle:  $D_1$  and  $D_3$  conduct: a-b-c-d.
- -ve 1/2 cycle:  $D_2$  and  $D_4$  conduct: d-b-c-a.
- $V_{DC} = \frac{2}{\pi} V_m \approx 64\% V_m$ .  
Peak-inverse voltage seen by each diode =  $V_m$ .

- Disadvantages:

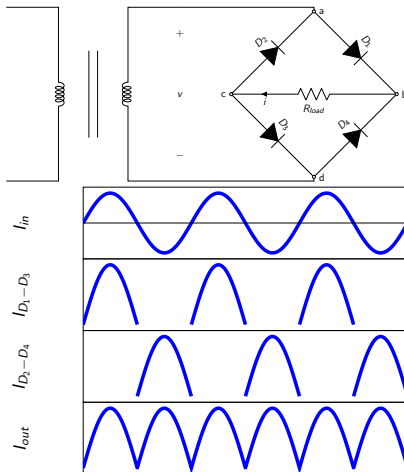- Needs 4 diodes.
- Power is dissipated in 2 of the 4 diodes at all times.
- Loses two diode drops in each direction.





# Full-Wave Rectifiers

Materials used here are bound by Fair Use for educational purpose.


## • Bridge rectifier:

- +ve 1/2 cycle:  $D_1$  and  $D_3$  conduct: a-b-c-d.
- -ve 1/2 cycle:  $D_2$  and  $D_4$  conduct: d-b-c-a.
- $V_{DC} = \frac{2}{\pi} V_m \approx 64\% V_m$ .  
Peak-inverse voltage seen by each diode =  $V_m$ .
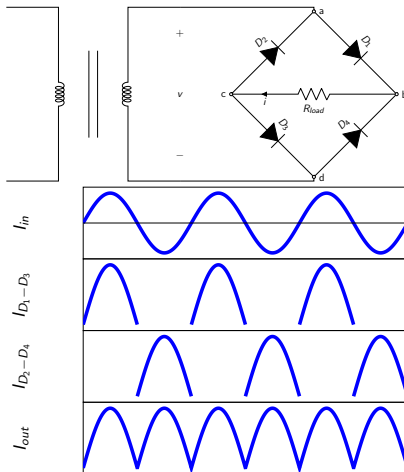
## • Disadvantages:

- Needs 4 diodes.
- Power is dissipated in 2 of the 4 diodes at all times.
- Loses two diode drops in each direction.


$$\eta = \left( \frac{V_{dc}}{V_{rms}} \right)^2 = \frac{8}{\pi^2} \approx 80\%$$


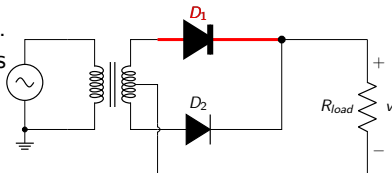
# Center-tapped full-wave rectifier

Materials used here are bound by Fair Use for educational purpose.

- +ve 1/2 cycle:  $D_1$  conducts.  
Top half of the transformer's secondary winding carries current.




# Center-tapped full-wave rectifier

Materials used here are bound by Fair Use for educational purpose.

- +ve 1/2 cycle:  $D_1$  conducts.  
Top half of the transformer's secondary winding carries current.

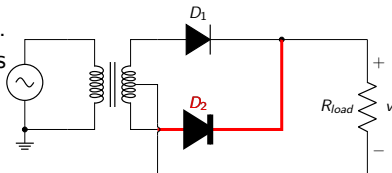
- -ve 1/2 cycle:  $D_2$  conducts.  
Bottom half of the transformer's secondary winding carries current.


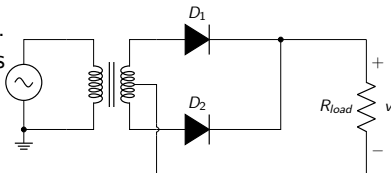
# Center-tapped full-wave rectifier

Materials used here are bound by Fair Use for educational purpose.

- +ve 1/2 cycle:  $D_1$  conducts. Top half of the transformer's secondary winding carries current.



- -ve 1/2 cycle:  $D_2$  conducts. Bottom half of the transformer's secondary winding carries current.
- Peak inverse voltage in each diode  $= 2V_m$ .

$$V_{DC} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t) = \frac{2}{\pi} V_m$$


$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 \, d(\omega t)} = \frac{V_m}{\sqrt{2}}$$

$$\eta = \left( \frac{V_{dc}}{V_{rms}} \right)^2 = \frac{8}{\pi^2} \approx 80\%$$
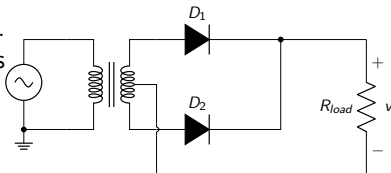
# Center-tapped full-wave rectifier

Materials used here are bound by Fair Use for educational purpose.

- +ve 1/2 cycle:  $D_1$  conducts. Top half of the transformer's secondary winding carries current.



- -ve 1/2 cycle:  $D_2$  conducts. Bottom half of the transformer's secondary winding carries current.

- Peak inverse voltage in each diode  $= 2V_m$ .

- 2 diodes needed. Less power dissipation / higher efficiency. More expensive transformer needed (generally found only in low-power applications).

$$V_{DC} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t) = \frac{2}{\pi} V_m$$

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 \, d(\omega t)} = \frac{V_m}{\sqrt{2}}$$

$$\eta = \left( \frac{V_{dc}}{V_{rms}} \right)^2 = \frac{8}{\pi^2} \approx 80\%$$


# Rectification

Materials used here are bound by Fair Use for educational purpose.

- Counting DC o/p from every  $360^\circ$  of input. Half-wave rectifier: 1-pulse. Full-wave rectifier: 2-pulse.
- Ripple voltage: AC voltage superposed on rectifier pure DC output. Undesirable.
- Can be reduced through filtering for low power.
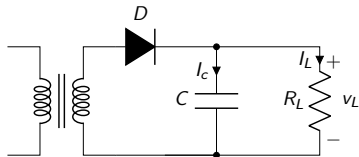
# Capacitor filter with half-wave rectifier


Materials used here are bound by Fair Use for educational purpose.



$$\tau = R_L C \gg T$$

$$V_r = \frac{\Delta q}{C} \approx \frac{I_{dc} T}{C}$$

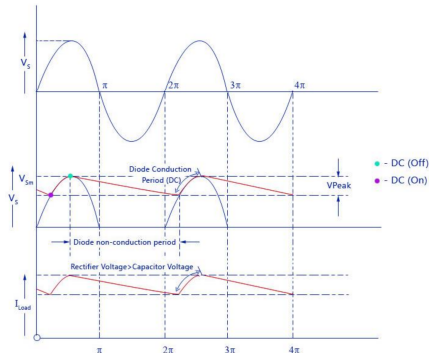
$$= \frac{I_{dc}}{fC} = \frac{V_{dc}}{fR_L C} = \frac{V_{dc}}{f\tau}$$



Output voltage remains almost constant
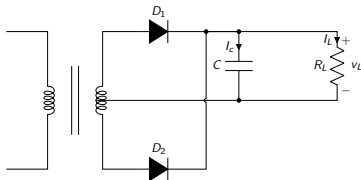
# Capacitor filter with full-wave rectifier

Materials used here are bound by Fair Use for educational purpose.




Discharge time is halved ( $T/2$ ).

$$\tau = R_L C \gg T$$

$$V_r = \frac{\Delta q}{C} \approx \frac{I_{dc} T}{2C}$$


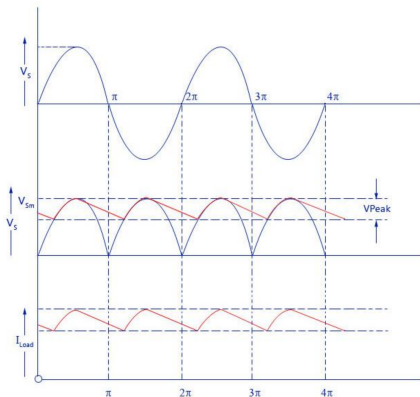
$$= \frac{I_{dc}}{2fC} = \frac{V_{dc}}{2fR_L C} = \frac{V_{dc}}{2f\tau}$$





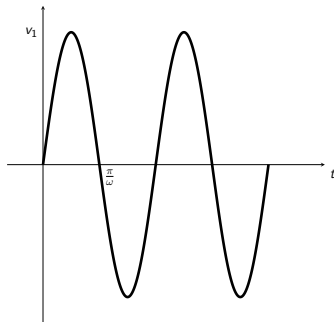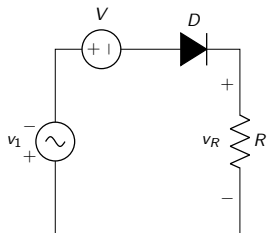
# Waveshaping circuits: clipper

Materials used here are bound by Fair Use for educational purpose.



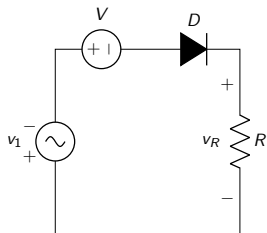
# Waveshaping circuits: clipper

Materials used here are bound by Fair Use for educational purpose.




$$v_1 = V + v_D + v_R$$

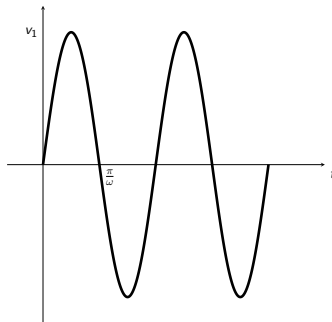

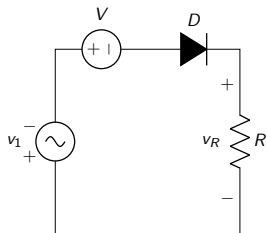
# Waveshaping circuits: clipper

Materials used here are bound by Fair Use for educational purpose.




$$v_1 = V + v_D + v_R$$

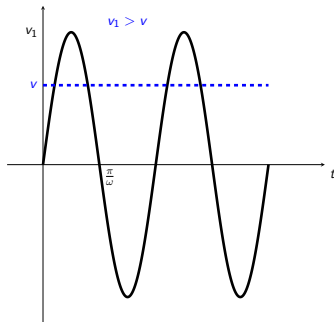- $v_1 \geq V$ :  $v_R = v_1 - V$  (diode conducts).



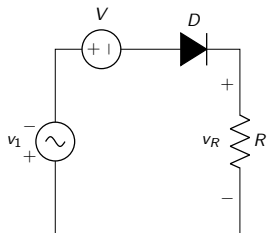
# Waveshaping circuits: clipper

Materials used here are bound by Fair Use for educational purpose.




$$v_1 = V + v_D + v_R$$

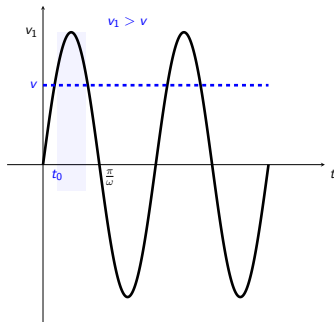- $v_1 \geq V$ :  $v_R = v_1 - V$  (diode conducts).
- $v_1 < V$ :  $v_R = 0$  (diode is off)



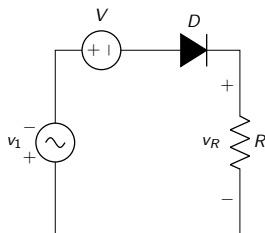
# Waveshaping circuits: clipper

Materials used here are bound by Fair Use for educational purpose.




$$v_1 = V + v_D + v_R$$

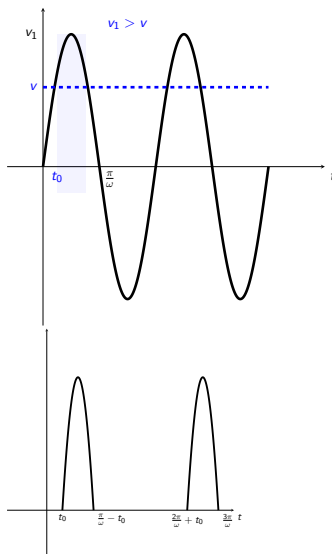- $v_1 \geq V$ :  $v_R = v_1 - V$  (diode conducts).
- $v_1 < V$ :  $v_R = 0$  (diode is off)



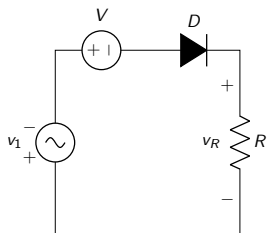
# Waveshaping circuits: clipper

Materials used here are bound by Fair Use for educational purpose.



$$v_1 = V + v_D + v_R$$

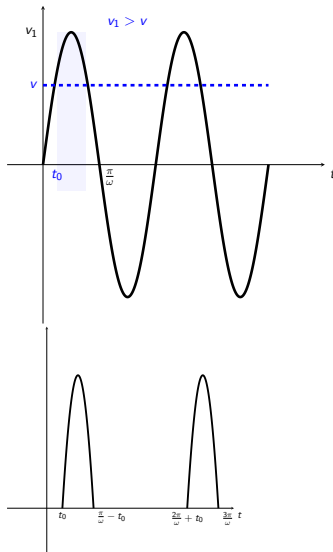
- $v_1 \geq V$ :  $v_R = v_1 - V$  (diode conducts).
- $v_1 < V$ :  $v_R = 0$  (diode is off)




Negative clipper
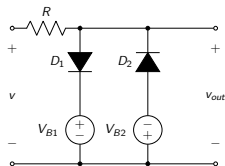
# Two-way clipping

Materials used here are bound by Fair Use for educational purpose.




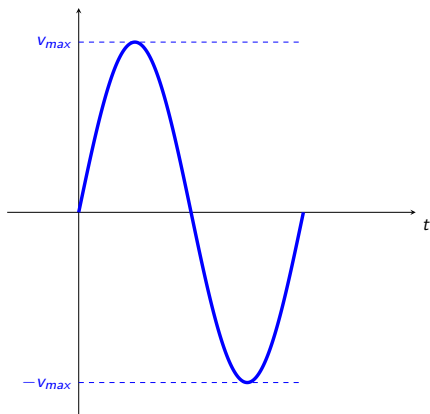- To get an undistorted signal to  $v_{out}$ , both  $D_1$  and  $D_2$  branches need to be open circuited.
- $D_1$  is FB when  $V > V_{B1}$ .
- $D_2$  is FB when  $V < -V_{B2}$ .



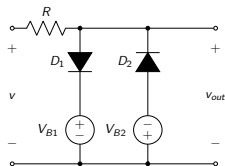
# Two-way clipping

Materials used here are bound by Fair Use for educational purpose.



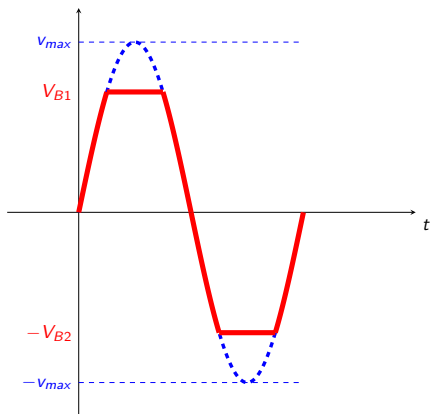
- To get an undistorted signal to  $v_{out}$ , both  $D_1$  and  $D_2$  branches need to be open circuited.
- $D_1$  is FB when  $V > V_{B1}$ .
- $D_2$  is FB when  $V < -V_{B2}$ .
- Outside of  $[-V_{B2}, V_{B1}]$ , voltage is clipped to the voltage in the respective branch.





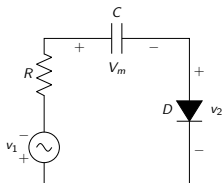
# Waveshaping circuits: clamping

Materials used here are bound by Fair Use for educational purpose.




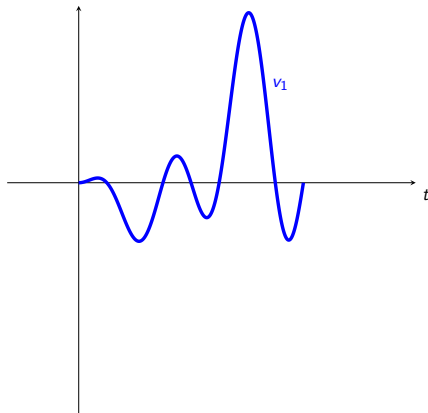- Clamping: “lock” or clamp the +ve or -ve peak to a pre-determined value.
- In the circuit,



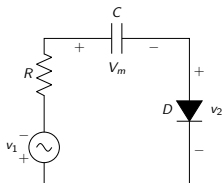
# Waveshaping circuits: clamping

Materials used here are bound by Fair Use for educational purpose.




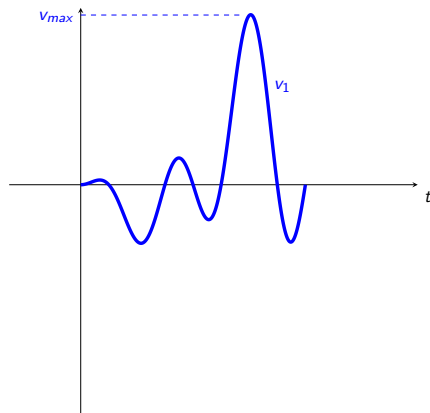- Clamping: “lock” or clamp the +ve or -ve peak to a pre-determined value.
- In the circuit,
  - For small  $R$ , capacitor charges quickly to peak value of  $v_1$  ( $V_m$ ).



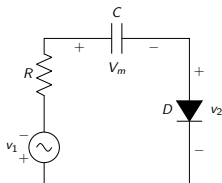
# Waveshaping circuits: clamping

Materials used here are bound by Fair Use for educational purpose.




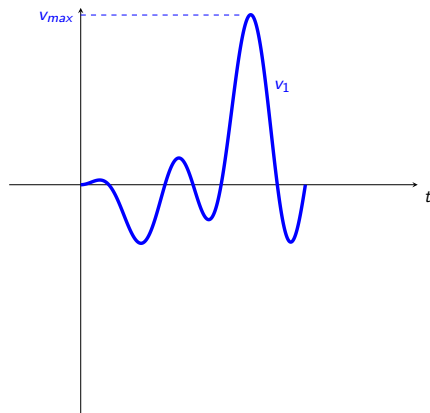- Clamping: “lock” or clamp the +ve or -ve peak to a pre-determined value.
- In the circuit,
  - For small  $R$ , capacitor charges quickly to peak value of  $v_1$  ( $V_m$ ).
  - For smaller values of input voltage, capacitor is “stuck” without a discharge path (except for tiny RB leakage through  $D$ ).



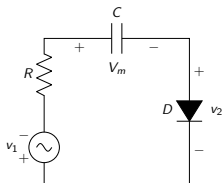
# Waveshaping circuits: clamping

Materials used here are bound by Fair Use for educational purpose.




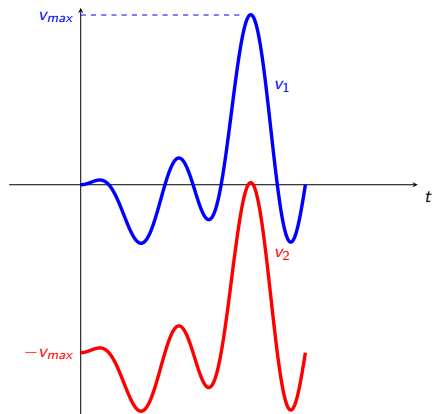- Clamping: “lock” or clamp the +ve or -ve peak to a pre-determined value.
- In the circuit,
  - For small  $R$ , capacitor charges quickly to peak value of  $v_1$  ( $V_m$ ).
  - For smaller values of input voltage, capacitor is “stuck” without a discharge path (except for tiny RB leakage through  $D$ ).
  - $v_2 \approx v_1 - V_m$ .



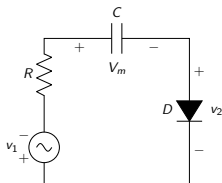
# Waveshaping circuits: clamping

Materials used here are bound by Fair Use for educational purpose.



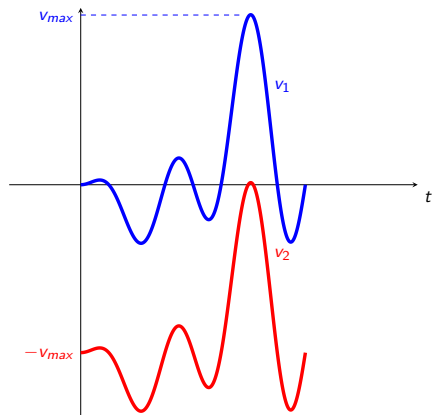- Clamping: “lock” or clamp the +ve or -ve peak to a pre-determined value.
- In the circuit,
  - For small  $R$ , capacitor charges quickly to peak value of  $v_1$  ( $V_m$ ).
  - For smaller values of input voltage, capacitor is “stuck” without a discharge path (except for tiny RB leakage through  $D$ ).
  - $v_2 \approx v_1 - V_m$ .




- Effect: shifting the AC signal by an amount dependent on its magnitude.
- Clamp down circuit. To clamp-up, flip diode.

# Waveshaping circuits: peak detector

Materials used here are bound by Fair Use for educational purpose.

- Peak detector.

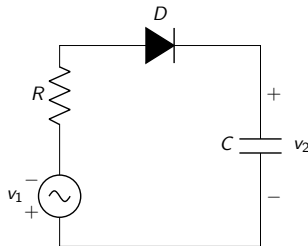

# Waveshaping circuits: peak detector

Materials used here are bound by Fair Use for educational purpose.

- Peak detector.
- Peak to peak detector.

